

LAB 9-10 - NANOPROCESSOR DESIGN COMPETITION

GROUP 89

- K.S. RANASINGHE - 210518H
- W.A.R.T FONSEKA - 210170G

LAB TASK

- Design a 4-bit arithmetic unit that can add and subtract signed integers.
- Design k-way b-bit multiplexers as necessary.
- Develop an assembly code that would simulate the necessary process.
- Hard code the Assembly code into the Program ROM.
- Design an Instruction Decoder that decodes the instructions in the Program ROM.
- Connect the individual components that were designed earlier together to create a Nano processor.

ASSEMBLY PROGRAM

```
MOVI      R7, 0      // move zero to register R7
MOVI      R1, 3      // move three to register R1
MOVI      R2, -1     // move negative one to register R2
ADD        R7, R1     // add values in R7 and R1 and move new value to R7
ADD        R1, R2     // add values in R1 and R2 and move new value to R1
JZR        R1, 7      // if value in R1 is equal to zero jump to instruction no. 7
JZR        R0, 3      // if value in R0 is equal to zero jump to instruction no. 3
END
```

MACHINE CODE REPRESENTATION

```
signal program_ROM : rom_type := (  
    "101110000000", --0  
    "100010000011", --1  
    "100100001111", --2  
    "001110010000", --3  
    "000010100000", --4  
    "110010000111", --5  
    "110000000011", --6  
    "100000000000" --7
```

VHDL CODES

- 4-bit Add/Subtract unit

Design Source File

```
entity AdderSubtractor is  
    Port ( A,B : in STD_LOGIC_VECTOR(3 downto 0);  
          C_in, Ctrl : in STD_LOGIC;  
          S : out STD_LOGIC_VECTOR(3 downto 0);  
          C_out, Zero, Overflow : out STD_LOGIC);  
end AdderSubtractor;  
  
architecture Behavioral of AdderSubtractor is  
    component FA  
        port(  
            A : in std_logic;  
            B : in std_logic;  
            C_in : in std_logic;  
            S : out std_logic;  
            C_out : out std_logic);  
    end component;  
  
    SIGNAL FA_C, FA_S, T : std_logic_vector(3 downto 0);  
    SIGNAL N : std_logic;
```

```

begin
  process(Ctrl, B)
  begin
    case Ctrl is
      when '1' => T <= NOT B;
      when '0' => T <= B;
      when others => T <= "UUUU";
    end case;
  end process;

  FA_0 :FA
  PORT MAP(
    A => A(0),
    B => T(0),
    C_in => Ctrl,
    S => FA_S(0),
    C_Out => FA_C(0));

  FA_1 :FA
  PORT MAP(
    A => A(1),
    B => T(1),
    C_in => FA_C(0),
    S => FA_S(1),
    C_Out => FA_C(1));

  FA_2 :FA
  PORT MAP(
    A => A(2),
    B => T(2),
    C_in => FA_C(1),
    S => FA_S(2),
    C_Out => FA_C(2));

  FA_3 :FA
  PORT MAP(
    A => A(3),
    B => T(3),
    C_in => FA_C(2),
    S => FA_S(3),
    C_Out => FA_C(3));

  S <= FA_S;
  C_out <= FA_C(3);

  N <= NOT (A(3) XOR B(3)) AND (NOT Ctrl) AND FA_C(3);
  Overflow <= A(3) AND T(3);

```

```

process(FA_S)
begin
    if FA_S = "0000" AND N = '0' then
        Zero <= '1';
    else
        Zero <= '0';
    end if;
end process;
end Behavioral;

```

Test Bench File

```

entity AdderSubtractorSim is
-- Port ( );
end AdderSubtractorSim;

architecture Behavioral of AdderSubtractorSim is
COMPONENT AdderSubtractor
    PORT( A,B : IN STD_LOGIC_VECTOR(3 downto 0);
          C_in, Ctrl : IN STD_LOGIC;
          S : OUT STD_LOGIC_VECTOR(3 downto 0);
          C_out, Zero, Overflow : OUT STD_LOGIC);
END COMPONENT;

SIGNAL A,B : std_logic_vector(3 downto 0);
SIGNAL C_in, Ctrl : std_logic;
SIGNAL S :std_logic_vector(3 downto 0);
SIGNAL C_out,Zero,Overflow : std_logic;

begin
    UUT : AdderSubtractor PORT MAP(
        A => A,
        B => B,
        Ctrl => Ctrl,
        C_in => C_in,
        C_out => C_out,
        Zero => Zero,
        Overflow => Overflow,
        S => S
    );

    process
    begin
        A <= "0000";
        B <= "0000";
    end process;

```

```
C_in <= '0';
Ctrl <= '0';

-- 0101 + 1011
WAIT FOR 100 ns;
A <= "0101";
B <= "1011";
Ctrl <= '1';

-- 0111 + 1111
WAIT FOR 100 ns;
A <= "0111";
B <= "1111";
Ctrl <= '0';

-- Index Number: 210518H => 11 0011 0110 0101 0110
-- Index Number: 210170G => 11 0011 0100 1111 1010

-- 0110 + 0101
WAIT FOR 100 ns;
A <= "0110";
B <= "0101";
Ctrl <= '0';

-- 0110 - 0011
WAIT FOR 100 ns;
A <= "0110";
B <= "0011";
Ctrl <= '1';

-- 1010 + 1111
WAIT FOR 100 ns;
A <= "1010";
B <= "1111";
Ctrl <= '0';

-- 0011 - 0100
WAIT FOR 100 ns;
A <= "0011";
B <= "0100";
Ctrl <= '1';

-- 0011 + 0011
WAIT FOR 100 ns;
A <= "0011";
B <= "0011";
Ctrl <= '0';

-- 0110 - 0100
```

```

        WAIT FOR 100 ns;
        A <= "0110";
        B <= "0100";
        Ctrl <= '1';

-- 0101 + 1111
        WAIT FOR 100 ns;
        A <= "0101";
        B <= "1111";
        Ctrl <= '0';

-- 0110 - 1010
        WAIT FOR 100 ns;
        A <= "0110";
        B <= "1010";
        Ctrl <= '1';

        WAIT;
    end process;

```

- 3-bit adder

Design Source File

```

entity Adder3Bit is
    Port ( A : in STD_LOGIC_VECTOR(2 downto 0);
          S : out STD_LOGIC_VECTOR(2 downto 0));
end Adder3Bit;

architecture Behavioral of Adder3Bit is

    SIGNAL T : std_logic_vector(2 downto 0);

begin

    T(0) <= '1';
    S(0) <= A(0) XOR T(0);

    T(1) <= A(0) AND T(0);
    S(1) <= A(1) XOR T(1);

    T(2) <= A(1) AND T(1);
    S(2) <= A(2) XOR T(2);

end Behavioral;

```

Test Bench File

```
entity Adder3BitSim is
-- Port ( );
end Adder3BitSim;

architecture Behavioral of Adder3BitSim is
  COMPONENT Adder3Bit
    PORT( A : IN STD_LOGIC_VECTOR(2 downto 0);
          S : OUT STD_LOGIC_VECTOR(2 downto 0));
  END COMPONENT;

  SIGNAL A : std_logic_vector(2 downto 0);
  SIGNAL S :std_logic_vector(2 downto 0);

begin
  UUT : Adder3Bit PORT MAP(
    A => A,
    S => S
  );
  process
  begin
    A <= "000";

    WAIT FOR 100 ns;
    A <= "001";

    WAIT FOR 100 ns;
    A <= "010";

    WAIT FOR 100 ns;
    A <= "011";

    WAIT FOR 100 ns;
    A <= "100";

    WAIT FOR 100 ns;
    A <= "101";

    WAIT FOR 100 ns;
    A <= "110";

    WAIT FOR 100 ns;
    A <= "111";
```

```
-- Index Number: 210518H => 110 011 011 001 010 110
-- Index Number: 210170G => 110 011 010 011 111 010
```

```
WAIT FOR 100 ns;
A <= "110";
```

```
WAIT FOR 100 ns;
A <= "010";
```

```
WAIT FOR 100 ns;
A <= "001";
```

```
WAIT FOR 100 ns;
A <= "011";
```

```
WAIT FOR 100 ns;
A <= "011";
```

```
WAIT FOR 100 ns;
A <= "110";
```

```
WAIT FOR 100 ns;
A <= "010";
```

```
WAIT FOR 100 ns;
A <= "111";
```

```
WAIT FOR 100 ns;
A <= "011";
```

```
WAIT FOR 100 ns;
A <= "010";
```

```
WAIT FOR 100 ns;
A <= "011";
```

```
WAIT FOR 100 ns;
A <= "110";
```

```
WAIT;
end process;
end Behavioral;
```


- 3-bit Program Counter (PC)

Design Source File

```
entity ProgramCounter is
  Port ( D : in STD_LOGIC_VECTOR(2 downto 0);
        Res, Clk : in STD_LOGIC;
        Q : out STD_LOGIC_VECTOR (2 downto 0));
end ProgramCounter;

architecture Behavioral of ProgramCounter is
  component D_FF
  port (
    D : in STD_LOGIC;
    Res : in STD_LOGIC;
    Clk : in STD_LOGIC;
    Q : out STD_LOGIC;
    Qbar : out STD_LOGIC );
  end component;

  component Slow_Clk
  port (
    Clk_in : in STD_LOGIC;
    Clk_out : out STD_LOGIC );
  end component;

  signal QD : std_logic_vector(2 downto 0);
  signal Clk_slow : std_logic;
begin
  Slow_Clk0 : Slow_Clk
  port map (
    Clk_in => Clk,
    Clk_out => Clk_slow );

  D_FF0 : D_FF
  port map (
    D => D(0),
    Res => Res,
    Clk => Clk_slow,
    Q => QD(0) );

  D_FF1 : D_FF
  port map (
    D => D(1),
    Res => Res,
    Clk => Clk_slow,
```

```

        Q => QD(1) );

D_FF2 : D_FF
port map (
    D => D(2),
    Res => Res,
    Clk => Clk_slow,
    Q => QD(2) );

Q <= QD;

end Behavioral;

```

Test Bench File

```

entity ProgramCounterSim is
-- Port ( );
end ProgramCounterSim;

architecture Behavioral of ProgramCounterSim is
COMPONENT ProgramCounter
    PORT( Res, Clk : IN STD_LOGIC;
          D : IN STD_LOGIC_VECTOR(2 downto 0);
          Q : OUT STD_LOGIC_VECTOR(2 DOWNTO 0));
END COMPONENT;

SIGNAL Res, Clk : std_logic;
SIGNAL D, Q : std_logic_vector(2 downto 0);

begin
    UUT : ProgramCounter PORT MAP(
        D => D,
        Res => Res,
        Clk => Clk,
        Q => Q );

    Clock : process
    begin
        Clk <= '0';
        WAIT FOR 1 ns;
    end process;
end Behavioral;

```

```

    Clk <= '1';
    WAIT FOR 1 ns;
end process;
--INPUT SIGNAL = 100MHz (10 ns)
--SLOW CLOCK COUNT = 50 000 000 == 50_000_000
--SLOW CLOCK SIM = WAIT FOR 1 ns
--OUTPUT SIGNAL = 0.2Hz (2 s)
process
begin
    D <= "000";
    Res <= '0';
    WAIT FOR 500 ns;
-- Index Number: 210518H => 110 011 011 001 010 110

    D <= "110";
    Res <= '1';
    WAIT FOR 5 ms;

    D <= "010";
    Res <= '0';
    WAIT FOR 5 ms;

    D <= "001";
    Res <= '1';
    WAIT FOR 5 ms;

    D <= "011";
    Res <= '0';
    WAIT FOR 4 ms;

    D <= "011";
    Res <= '1';
    WAIT FOR 5 ms;

-- Index Number: 210170G => 110 011 010 011 111 010

    D <= "010";
    Res <= '0';
    WAIT FOR 7 ms;

    D <= "111";
    Res <= '1';
    WAIT FOR 5 ms;

    D <= "011";
    Res <= '0';
    WAIT FOR 3 ms;

    D <= "010";

```

```

Res <= '1';
WAIT FOR 5 ms;

D <= "011";
Res <= '0';
WAIT FOR 2 ms;

end process;
end Behavioral;

```

- 2-way 3-bit multiplexer

Design Source File

```

entity Mux_2way_3bit is
  Port ( Sel,Clk : in STD_LOGIC;
        A,B : in STD_LOGIC_VECTOR (2 downto 0);
        Y : out STD_LOGIC_VECTOR(2 downto 0));
end Mux_2way_3bit;

architecture Behavioral of Mux_2way_3bit is

begin
  process(Clk,Sel)
  begin
    if (rising_edge(Clk)) then
      case Sel is
        when '0' => Y <= A;
        when '1' => Y <= B;
        when others => Y <= "UUU";
      end case;
    end if;
  end process;

end Behavioral;

```

Test Bench File

```
entity Mux2Sim is
-- Port ( );
end Mux2Sim;

architecture Behavioral of Mux2Sim is
COMPONENT Mux_2way_3bit
  PORT( Sel,Clk : IN STD_LOGIC;
        A,B : IN STD_LOGIC_VECTOR(2 DOWNTO 0);
        Y : OUT STD_LOGIC_VECTOR(2 DOWNTO 0));
END COMPONENT;

SIGNAL Sel,Clk : std_logic;
SIGNAL A,B,Y : std_logic_vector(2 downto 0);

begin
  UUT : Mux_2way_3bit PORT MAP(
    Sel => Sel,
    A => A,
    B => B,
    Y => Y,
    Clk => Clk);

  Clock : process
  begin
    Clk <= '0';
    WAIT FOR 1 ns;

    Clk <= '1';
    WAIT FOR 1 ns;
  end process;

  process
  begin
    -- Index Number: 210518H => 110 011 011 001 010 110
    -- Index Number: 210170G => 110 011 010 011 111 010

    Sel <= '0';
    A <= "110";
    B <= "010";
    WAIT FOR 50 ns;

    Sel <= '1';
    WAIT FOR 50 ns;

    Sel <= '0';
```

```
A <= "010";  
B <= "111";  
WAIT FOR 50 ns;
```

```
Sel <= '0';  
A <= "001";  
B <= "011";  
WAIT FOR 50 ns;
```

```
Sel <= '1';  
WAIT FOR 50 ns;
```

```
Sel <= '0';  
A <= "011";  
B <= "010";  
WAIT FOR 50 ns;
```

```
Sel <= '1';  
WAIT FOR 50 ns;
```

```
Sel <= '0';  
A <= "011";  
B <= "011";  
WAIT FOR 50 ns;
```

```
Sel <= '1';  
WAIT FOR 50 ns;
```

```
Sel <= '0';  
A <= "110";  
B <= "110";  
WAIT FOR 50 ns;
```

```
Sel <= '1';  
WAIT FOR 50 ns;
```

```
end process;  
end Behavioral;
```

- 2-way 4-bit multiplexer

Design Source File

```
entity Mux_2way_4bit is
  Port ( Sel, Clk : in STD_LOGIC;
        A,B : in STD_LOGIC_VECTOR (3 downto 0);
        Y : out STD_LOGIC_VECTOR(3 downto 0));
end Mux_2way_4bit;

architecture Behavioral of Mux_2way_4bit is

begin

  process(Clk,Sel)
  begin
    if (rising_edge(Clk)) then
      case Sel is
        when '0' => Y <= A;
        when '1' => Y <= B;
        when others => Y <= "UUUU";
      end case;
    end if;
  end process;

end Behavioral;
```

Test Bench File

```
entity Mux1Sim is
-- Port ( );
end Mux1Sim;

architecture Behavioral of Mux1Sim is
  COMPONENT Mux_2way_4bit
    PORT( Sel, Clk : IN STD_LOGIC;
          A,B : IN STD_LOGIC_VECTOR(3 DOWNT0 0);
          Y : OUT STD_LOGIC_VECTOR(3 DOWNT0 0));
  END COMPONENT;

  SIGNAL Sel,Clk : std_logic;
  SIGNAL A,B,Y : std_logic_vector(3 downto 0);

begin
  UUT : Mux_2way_4bit PORT MAP(
```

```

Sel => Sel,
A => A,
B => B,
Y => Y,
Clk => Clk);
Clock : process
begin
  Clk <= '0';
  WAIT FOR 1 ns;
  Clk <= '1';
  WAIT FOR 1 ns;
end process;
process
begin
  -- Index Number: 210518H => 11 0011 0110 0101 0110
  -- Index Number: 210170G => 11 0011 0100 1111 1010
  Sel <= '0';
  A <= "0110";
  B <= "1010";
  WAIT FOR 50 ns;

  Sel <= '1';
  WAIT FOR 50 ns;

  Sel <= '0';
  A <= "0101";
  B <= "1111";
  WAIT FOR 50 ns;

  Sel <= '1';
  WAIT FOR 50 ns;

  Sel <= '0';
  A <= "0110";
  B <= "0100";
  WAIT FOR 50 ns;

  Sel <= '1';
  WAIT FOR 50 ns;

  Sel <= '0';
  A <= "0011";
  B <= "0011";
  WAIT FOR 50 ns;

  Sel <= '1';
  WAIT FOR 50 ns;
end process;
end Behavioral;
```


- 8-way 4-bit multiplexer

Design Source File

```
entity Mux_8way_4bit is
  Port ( Clk : in STD_LOGIC;
        Sel : in STD_LOGIC_VECTOR (2 downto 0);
        A,B,C,D,E,F,G,H : in STD_LOGIC_VECTOR (3 downto 0);
        Y : out STD_LOGIC_VECTOR(3 downto 0));
end Mux_8way_4bit;

architecture Behavioral of Mux_8way_4bit is

begin

  process(Clk,Sel)
  begin
    if (rising_edge(Clk)) then
      case Sel is
        when "000" => Y <= A;
        when "001" => Y <= B;
        when "010" => Y <= C;
        when "011" => Y <= D;
        when "100" => Y <= E;
        when "101" => Y <= F;
        when "110" => Y <= G;
        when "111" => Y <= H;
        when others => Y <= "UUUU";
      end case;
    end if;

  end process;
end Behavioral;
```

Test Bench File

```
entity MuxSim is
-- Port ( );
end MuxSim;

architecture Behavioral of MuxSim is

COMPONENT Mux_8way_4bit
PORT( Clk : IN STD_LOGIC;
      Sel : IN STD_LOGIC_VECTOR(2 DOWNTO 0);
      A,B,C,D,E,F,G,H : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
      Y : OUT STD_LOGIC_VECTOR(3 DOWNTO 0));
END COMPONENT;

SIGNAL Clk : std_logic;
SIGNAL Sel : std_logic_vector(2 downto 0);
SIGNAL A,B,C,D,E,F,G,H,Y : std_logic_vector(3 downto 0);

begin

UUT : Mux_8way_4bit PORT MAP(
  Sel => Sel,
  Clk => Clk,
  A => A,
  B => B,
  C => C,
  D => D,
  E => E,
  F => F,
  G => G,
  H => H,
  Y => Y );

Clock : process
begin
  Clk <= '0';
  WAIT FOR 1 ns;

  Clk <= '1';
  WAIT FOR 1 ns;
end process;

process
begin
```

```
Sel <= "000";

A <= "0110";

B <= "1001";

C <= "1010";

D <= "0101";

E <= "0110";

F <= "1101";

G <= "1110";

H <= "1111";

WAIT FOR 50 ns;

-- Index Number: 210518H => 110 011 011 001 010 110

Sel <= "110";
WAIT FOR 50 ns;

Sel <= "010";
WAIT FOR 50 ns;

Sel <= "001";
WAIT FOR 50 ns;

Sel <= "011";
WAIT FOR 50 ns;

Sel <= "011";
WAIT FOR 50 ns;

Sel <= "110";
WAIT FOR 50 ns;

-- Index Number: 210170G => 110 011 010 011 111 010

Sel <= "010";
WAIT FOR 50 ns;

Sel <= "111";
WAIT FOR 50 ns;
```

```

Sel <= "011";
WAIT FOR 50 ns;

Sel <= "010";
WAIT FOR 50 ns;

Sel <= "011";
WAIT FOR 50 ns;

Sel <= "110";
WAIT FOR 50 ns;

end process;
end Behavioral;

```

- **Register Bank**

Design Source File

```

entity RegisterBank is
  Port ( D : in STD_LOGIC_VECTOR(3 downto 0);
        RegSel : in STD_LOGIC_VECTOR(2 downto 0);
        Res : in STD_LOGIC;
        Clk : in STD_LOGIC;
        R0, R1, R2, R3, R4, R5, R6, R7 : out STD_LOGIC_VECTOR(3 downto 0));
end RegisterBank;

architecture Behavioral of RegisterBank is
  component D_FF_4bit
    port (
      D : in STD_LOGIC_VECTOR(3 downto 0);
      Res : in STD_LOGIC;
      En : in STD_LOGIC;
      Clk : in STD_LOGIC;
      Q : out STD_LOGIC_VECTOR(3 downto 0));
  end component;

```

```
component Slow_Clk is
Port ( Clk_in : in STD_LOGIC;
      Clk_out : out STD_LOGIC);
end component;

component Decoder_3_to_8 is
Port ( I : in STD_LOGIC_VECTOR (2 downto 0);
      EN : in STD_LOGIC;
      Y : out STD_LOGIC_VECTOR (7 downto 0));
end component;

signal T : STD_LOGIC_VECTOR(7 downto 0);
signal Clk_slow : STD_LOGIC;
```

```
begin
```

```
Slow_Clk_0 : Slow_Clk
port map(
  Clk_in => Clk,
  Clk_out => Clk_slow );
```

```
Decoder_3_to_8_0 : Decoder_3_to_8
port map(
  I => RegSel,
  EN => '1',
  Y => T );
```

```
R0 <= "0000";
```

```
R_1 : D_FF_4bit
port map (
  D => D,
  Res => Res,
  En => T(1),
  Clk => Clk_slow,
  Q => R1 );
```

```
R_2 : D_FF_4bit
port map (
  D => D,
  Res => Res,
  En => T(2),
  Clk => Clk_slow,
  Q => R2 );
```

```
R_3 : D_FF_4bit
port map (
  D => D,
  Res => Res,
```

```
En => T(3),  
Clk => Clk_slow,  
Q => R3 );
```

```
R_4 : D_FF_4bit  
port map (  
  D => D,  
  Res => Res,  
  En => T(4),  
  Clk => Clk_slow,  
  Q => R4 );
```

```
R_5 : D_FF_4bit  
port map (  
  D => D,  
  Res => Res,  
  En => T(5),  
  Clk => Clk_slow,  
  Q => R5 );
```

```
R_6 : D_FF_4bit  
port map (  
  D => D,  
  Res => Res,  
  En => T(6),  
  Clk => Clk_slow,  
  Q => R6 );
```

```
R_7 : D_FF_4bit  
port map (  
  D => D,  
  Res => Res,  
  En => T(7),  
  Clk => Clk_slow,  
  Q => R7 );
```

```
end Behavioral;
```

Test Bench File

```
entity RegisterBankSim is
-- Port ( );
end RegisterBankSim;

architecture Behavioral of RegisterBankSim is
  COMPONENT RegisterBank
    PORT( D : IN STD_LOGIC_VECTOR(3 downto 0);
          RegSel : IN STD_LOGIC_VECTOR(2 downto 0);
          Res, Clk : IN STD_LOGIC;
          R0, R1, R2, R3, R4, R5, R6, R7 : OUT STD_LOGIC_VECTOR(3 downto 0));
  END COMPONENT;

  SIGNAL D : std_logic_vector(3 downto 0);
  SIGNAL RegSel : std_logic_vector(2 downto 0);
  SIGNAL Res, Clk : std_logic;
  SIGNAL R0, R1, R2, R3, R4, R5, R6, R7 :std_logic_vector(3 downto 0) := "0000";

begin

  UUT : RegisterBank PORT MAP(
    D => D,
    RegSel => RegSel,
    Res => Res,
    Clk => Clk,
    R0 => R0,
    R1 => R1,
    R2 => R2,
    R3 => R3,
    R4 => R4,
    R5 => R5,
    R6 => R6,
    R7 => R7
  );

  Clock : process
  begin
    Clk <= '0';
    WAIT FOR 1 ns;

    Clk <= '1';
    WAIT FOR 1 ns;
  end process;

  --INPUT SIGNAL = 100MHz (10 ns)
  --SLOW CLOCK COUNT = 500 000 000 == 50_000_000
  --SLOW CLOCK SIM = WAIT FOR 1 ns
  --OUTPUT SIGNAL = 0.2Hz (2 s)
```

```
process
begin

    Res <= '1';
    WAIT FOR 5 ms;

    Res <= '0';
    D <= "0001";
    RegSel <= "000";
    WAIT FOR 5 ms;

    RegSel <= "001";
    WAIT FOR 5 ms;

    RegSel <= "010";
    WAIT FOR 5 ms;

    RegSel <= "011";
    WAIT FOR 5 ms;

    RegSel <= "100";
    WAIT FOR 5 ms;

    RegSel <= "101";
    WAIT FOR 5 ms;

    RegSel <= "110";
    WAIT FOR 5 ms;

    RegSel <= "111";
    WAIT FOR 5 ms;

    Res <= '1';
    RegSel <= "000";
    WAIT FOR 5 ms;

    RegSel <= "001";
    WAIT FOR 5 ms;

    RegSel <= "010";
    WAIT FOR 5 ms;

    RegSel <= "011";
    WAIT FOR 5 ms;

    RegSel <= "100";
    WAIT FOR 5 ms;
```



```
RegSel <= "101";  
WAIT FOR 5 ms;
```

```
RegSel <= "110";  
WAIT FOR 5 ms;
```

```
RegSel <= "111";  
WAIT FOR 5 ms;
```

```
-- Index Number: 210518H => 11 0011 0110 0101 0110  
-- Index Number: 210170G => 11 0011 0100 1111 1010
```

```
Res <= '0';  
D <= "0110";  
RegSel <= "000";  
WAIT FOR 5 ms;
```

```
D <= "0101";  
RegSel <= "001";  
WAIT FOR 5 ms;
```

```
D <= "0110";  
RegSel <= "010";  
WAIT FOR 5 ms;
```

```
D <= "0011";  
RegSel <= "011";  
WAIT FOR 5 ms;
```

```
Res <= '0';  
D <= "1010";  
RegSel <= "100";  
WAIT FOR 5 ms;
```

```
D <= "1111";  
RegSel <= "101";  
WAIT FOR 5 ms;
```

```
D <= "0100";  
RegSel <= "110";  
WAIT FOR 5 ms;
```

```
D <= "0011";  
RegSel <= "111";  
WAIT;
```

```
end process;  
end Behavioral;
```

- Program ROM

Design Source File

```
entity ProgramROM is
  Port ( Sel : in STD_LOGIC_VECTOR (2 downto 0);
        I : out STD_LOGIC_VECTOR (11 downto 0));
end ProgramROM;

architecture Behavioral of ProgramROM is
  type rom_type is array (0 to 7) of std_logic_vector(11 downto 0);

  signal program_ROM : rom_type := (
    "101110000000", --0
    "100010000011", --1
    "100100001111", --2
    "001110010000", --3
    "000010100000", --4
    "110010000111", --5
    "110000000011", --6
    "100000000000" --7

  );
begin
  I <= program_ROM(to_integer(unsigned(Sel)));

end Behavioral;
```

Test Bench File

```
entity ProgramROMSim is
-- Port ( );
end ProgramROMSim;

architecture Behavioral of ProgramROMSim is
  COMPONENT ProgramROM
    PORT( Sel : IN STD_LOGIC_VECTOR(2 downto 0);
          I : OUT STD_LOGIC_VECTOR(11 DOWNT0 0));
  END COMPONENT;

  SIGNAL Sel : std_logic_vector(2 downto 0);
  SIGNAL I : std_logic_vector(11 downto 0);
```

```
begin
UUT : ProgramROM PORT MAP(
    Sel => Sel,
    I => I );
process
begin
    -- Index Number: 210518H => 110 011 011 001 010 110
    Sel <= "110";
    WAIT FOR 5 ms;

    Sel <= "010";
    WAIT FOR 5 ms;

    Sel <= "001";
    WAIT FOR 5 ms;

    Sel <= "011";
    WAIT FOR 5 ms;

    -- Index Number: 210170G => 110 011 010 011 111 010
    Sel <= "010";
    WAIT FOR 5 ms;

    Sel <= "111";
    WAIT FOR 5 ms;

    Sel <= "011";
    WAIT FOR 5 ms;

    Sel <= "010";
    WAIT FOR 5 ms;

end process;
end Behavioral;
```

- Instruction Decoder

Design Source File

```
entity InstructionDecoder is
  Port ( JumpCheck : in STD_LOGIC;
        A : in STD_LOGIC_VECTOR (11 downto 0);
        Reg1, Reg2, Jump : out STD_LOGIC_VECTOR(2 downto 0);
        LoadSel, OpSel, Jflag : out STD_LOGIC;
        Val : out STD_LOGIC_VECTOR(3 downto 0));
end InstructionDecoder;

architecture Behavioral of InstructionDecoder is
  signal Op : std_logic_vector(1 downto 0);

begin
  Op <= A(11 downto 10);
  Reg1 <= A(9 downto 7);
  Reg2 <= A(6 downto 4);
  Val <= A(3 downto 0);
  Jump <= A(2 downto 0);

  process (Op,JumpCheck)
  begin

    case Op is
      when "00" => OpSel <= '0'; LoadSel <= '0'; Jflag <= '0';
      when "01" => OpSel <= '1'; LoadSel <= '0'; Jflag <= '0';
      when "10" => LoadSel <= '1'; OpSel <= '0'; Jflag <= '0';
      when "11" =>
        case JumpCheck is
          when '1' => Jflag <= '1'; OpSel <= '0'; LoadSel <= '0';
          when others => Jflag <= '0'; OpSel <= '0'; LoadSel <= '0';
        end case;
      when others => Jflag <= '0'; OpSel <= '0'; LoadSel <= '0';
    end case;

  end process;

end Behavioral;
```

Test Bench File

```
entity InstructionDecoderSim is
-- Port ( );
end InstructionDecoderSim;

architecture Behavioral of InstructionDecoderSim is
  COMPONENT InstructionDecoder
    PORT( JumpCheck : in STD_LOGIC;
          A : IN STD_LOGIC_VECTOR(11 downto 0);
          Reg1, Reg2, Jump : OUT STD_LOGIC_VECTOR(2 DOWNTO 0);
          LoadSel, OpSel, Jflag : out STD_LOGIC;
          Val : out STD_LOGIC_VECTOR(3 downto 0));
  END COMPONENT;

  SIGNAL JumpCheck : std_logic;
  SIGNAL A : std_logic_vector(11 downto 0);
  SIGNAL Reg1, Reg2, Jump : std_logic_vector(2 downto 0);
  SIGNAL LoadSel, OpSel, Jflag : std_logic;
  SIGNAL Val : std_logic_vector(3 downto 0);

begin
  UUT : InstructionDecoder PORT MAP(
    JumpCheck => JumpCheck,
    A => A,
    Reg1 => Reg1,
    Reg2 => Reg2,
    Jump => Jump,
    LoadSel => LoadSel,
    OpSel => OpSel,
    Jflag => Jflag,
    Val => Val );

  process
  begin
    -- Index Number: 210518H => 11 0011 0110 0101 0110
    -- Index Number: 210170G => 11 0011 0100 1111 1010
    JumpCheck <= '0';
    A <= "011001010110";
    WAIT FOR 5 ms;

    A <= "001101100101";
    WAIT FOR 5 ms;

    A <= "110011011001";
    WAIT FOR 5 ms;

    JumpCheck <= '1';
    WAIT FOR 5 ms;
```

```

A <= "010011111010";
WAIT FOR 5 ms;

A <= "001101001111";
WAIT FOR 5 ms;

A <= "110011010011";
WAIT FOR 5 ms;

JumpCheck <= '0';
WAIT FOR 5 ms;

end process;
end Behavioral;

```

- Seven-Segment ROM (LUT)

Design Source File

```

entity LUT is
  Port ( address : in STD_LOGIC_VECTOR (3 downto 0);
        data : out STD_LOGIC_VECTOR (6 downto 0));
end LUT;

architecture Behavioral of LUT is
  type rom_type is array (0 to 15) of std_logic_vector(6 downto 0);

  signal sevenSegment_ROM : rom_type := (
    "1000000", --0
    "1111001", --1
    "0100100", --2
    "0110000", --3
    "0011001", --4
    "0010010", --5
    "0000010", --6
    "1111000", --7
    "0000000", --8
    "0010000", --9
    "0001000", --A
    "0000011", --B
    "1000110", --C
    "0100001", --D
    "0000110", --E
    "0001110" --F
  );
begin
  data <= sevenSegment_ROM(to_integer(unsigned(address)));
end Behavioral;

```

- Seven-Segment Display

Design Source File

```
entity Display is
  Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
        S_7Seg : out STD_LOGIC_VECTOR (6 downto 0));
end Display;

architecture Behavioral of Display is

  component LUT is
    Port ( address : in STD_LOGIC_VECTOR (3 downto 0);
          data : out STD_LOGIC_VECTOR (6 downto 0));
  end component;

begin

  LUT_1_0 : LUT
  port map(
    address => A,
    data => S_7Seg );

end Behavioral;
```

Test Bench File

```
entity DisplaySim is
-- Port ( );
end DisplaySim;

architecture Behavioral of DisplaySim is
  component Display is
    port (
      A : in std_logic_vector(3 downto 0);
      S_7Seg : out std_logic_vector(6 downto 0));

  end component;

  signal A : std_logic_vector(3 downto 0) := "0000";
  signal S_7Seg : std_logic_vector(6 downto 0);

begin
  UUT : Display PORT MAP (
    A => A,
    S_7Seg => S_7Seg
  );
end;
```

```
process
begin

    A <= "0000";
    wait for 5 ns;

    A <= "0001";
    wait for 5 ns;

    A <= "0010";
    wait for 5 ns;

    A <= "0011";
    wait for 5 ns;

    A <= "0100";
    wait for 5 ns;

    A <= "0101";
    wait for 5 ns;

    A <= "0110";
    wait for 5 ns;

    A <= "0111";
    wait for 5 ns;

    A <= "1000";
    wait for 5 ns;

    A <= "1001";
    wait for 5 ns;

    A <= "1010";
    wait for 5 ns;

    A <= "1011";
    wait for 5 ns;

    A <= "1100";
    wait for 5 ns;

    A <= "1101";
    wait for 5 ns;

    A <= "1110";
    wait for 5 ns;

    A <= "1111";
    wait;
    wait;
end process;
end Behavioral;
```


- Slow Clock

Design Source File

```
entity Slow_Clk is
  Port ( Clk_in : in STD_LOGIC;
        Clk_out : out STD_LOGIC);
end Slow_Clk;

architecture Behavioral of Slow_Clk is
  signal count : integer := 1;
  signal clk_status : std_logic := '0';

  begin
    process (Clk_in) begin
      if (rising_edge(Clk_in)) then
        count <= count + 1;
        if (count = 50_000_000) then
          clk_status <= not clk_status;
          Clk_out <= clk_status;
          count <= 1;
        end if;
      end if;
    end process;

  end Behavioral;
```

- Micro Processor

Design Source File

```
entity MicroProcessor is
  Port ( Res, Clk : in STD_LOGIC;
        S : out STD_LOGIC_VECTOR(3 downto 0);
        Zero, Overflow : out STD_LOGIC;
        S_7Seg : out STD_LOGIC_VECTOR (6 downto 0));

end MicroProcessor;

architecture Behavioral of MicroProcessor is
  component InstructionDecoder
    Port ( JumpCheck : in STD_LOGIC;
          A : in STD_LOGIC_VECTOR (11 downto 0);
          Reg1, Reg2, Jump : out STD_LOGIC_VECTOR(2 downto 0);
          LoadSel, OpSel, Jflag : out STD_LOGIC;
          Val : out STD_LOGIC_VECTOR(3 downto 0));
  end component;
```

```

component ProgramROM
Port ( Sel : in STD_LOGIC_VECTOR (2 downto 0);
      I : out STD_LOGIC_VECTOR (11 downto 0));
end component;

component ProgramCounter
Port ( D : in STD_LOGIC_VECTOR(2 downto 0);
      Res, Clk : in STD_LOGIC;
      Q : out STD_LOGIC_VECTOR (2 downto 0));
end component;

component Adder3Bit
Port ( A : in STD_LOGIC_VECTOR(2 downto 0);
      S : out STD_LOGIC_VECTOR(2 downto 0));
end component;

component Mux_2way_3bit
Port ( Sel, Clk : in STD_LOGIC;
      A, B : in STD_LOGIC_VECTOR (2 downto 0);
      Y : out STD_LOGIC_VECTOR(2 downto 0));
end component;

component Mux_2way_4bit
Port ( Sel, Clk : in STD_LOGIC;
      A, B : in STD_LOGIC_VECTOR (3 downto 0);
      Y : out STD_LOGIC_VECTOR(3 downto 0));
end component;

component Mux_8way_4bit
Port ( Clk : in STD_LOGIC;
      Sel : in STD_LOGIC_VECTOR (2 downto 0);
      A, B, C, D, E, F, G, H : in STD_LOGIC_VECTOR (3 downto 0);
      Y : out STD_LOGIC_VECTOR(3 downto 0));
end component;

component RegisterBank
Port ( D : in STD_LOGIC_VECTOR(3 downto 0);
      RegSel : in STD_LOGIC_VECTOR(2 downto 0);
      Res : in STD_LOGIC;
      Clk : in STD_LOGIC;
      R0, R1, R2, R3, R4, R5, R6, R7 : out STD_LOGIC_VECTOR(3 downto 0));
end component;

component AdderSubtractor
Port ( A, B : in STD_LOGIC_VECTOR(3 downto 0);
      C_in, Ctrl : in STD_LOGIC;
      S : out STD_LOGIC_VECTOR(3 downto 0);
      C_out, Zero, Overflow : out STD_LOGIC);
end component;

```

```

component Display
Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
      S_7Seg : out STD_LOGIC_VECTOR (6 downto 0));
end component;

SIGNAL Jflag, JumpCheck, LoadSel, OpSel : std_logic;
-- Jflag - this signal indicates whether a jump is called
-- JumpCheck - this signal checks whether register is empty to jump
-- LoadSel - this signal is sent to the 2 way 4 bit mux as the selector
-- OpSel - this signal is sent to the Adder Subtractor unit to select the operation

SIGNAL C_out : std_logic;
-- C_out - this is a internal signal generated by the Adder Subtractor unit indicating whether
there is carry out

SIGNAL T, R, R0, R1, R2, R3, R4, R5, R6, R7, M1, M2, D : std_logic_vector(3 downto 0);
-- T - this is 4 bit bus connecting Instruction Decoder to 2 way 4 bit mux
-- R - this is 4 bit bus connecting 2 way 4 bit mux to Register Bank
-- R(0-7) - these are 4 bit busses connecting the individual registers to the 8 way 4 bit mux
-- M1,M2 - these are 4 bit busses connecting the two 8 way 4 bit mux to the Adder Subtractor
unit
-- D - this is a 4 bit bus connecting the output of Adder Subtractor unit to 2 way 4 bit mux

SIGNAL Sel,P, A, J, RS1, RS2 : std_logic_vector(2 downto 0);
-- Sel - this is a 3 bit bus connecting Program Counter to Program ROM and 3 Bit Adder
-- P - this is a 3 bit bus connecting 2 way 3 bit mux to the Program Counter
-- A - this is a 3 bit bus connecting 3 bit Adder to 2 way 3 bit mux
-- J - this is a 3 bit bus connecting Instruction Decoder to 2 way 3 bit mux
-- RS1, RS2 - these are signals sent by Instruction Decoder to the two 8 way 4 bit mux as
selectors

SIGNAL I : std_logic_vector(11 downto 0);
-- I - this is a 12 bit bus connecting Program ROM to Instruction Decoder

begin
  IntructionDecoder_0 : InstructionDecoder
    PORT MAP(
      JumpCheck => JumpCheck,
      A => I,
      Reg1 => RS1,
      Reg2 => RS2,
      Jump => J,
      LoadSel => LoadSel,
      OpSel => OpSel,
      Jflag => Jflag,
      Val => T);

  ProgramROM_0 : ProgramROM
    PORT MAP(
      Sel => Sel,
      I => I);

```

```
ProgramCounter_0 : ProgramCounter
  PORT MAP(
    D => P,
    Res => Res,
    Clk => Clk,
    Q => Sel);
```

```
Adder3Bit_0 : Adder3Bit
  PORT MAP(
    A => Sel,
    S => A);
```

```
Mux_2way_3bit_0 : Mux_2way_3bit
  PORT MAP(
    Sel => Jflag,
    Clk => Clk,
    A => A,
    B => J,
    Y => P);
```

```
Mux_2way_4bit_0 : Mux_2way_4bit
  PORT MAP(
    Sel => LoadSel,
    Clk => Clk,
    A => D,
    B => T,
    Y => R);
```

```
RegisterBank_0 : RegisterBank
  PORT MAP(
    D => R,
    RegSel => RS1,
    Res => Res,
    Clk => Clk,
    R0 => R0,
    R1 => R1,
    R2 => R2,
    R3 => R3,
    R4 => R4,
    R5 => R5,
    R6 => R6,
    R7 => R7 );
```

```
Mux_8way_4bit_0 : Mux_8way_4bit
  PORT MAP(
    Sel => RS1,
    Clk => Clk,
    A => R0,
    B => R1,
    C => R2,
    D => R3,
    E => R4,
    F => R5,
```

```

    G => R6,
    H => R7,
    Y => M1);

Mux_8way_4bit_1 : Mux_8way_4bit
PORT MAP(
    Sel => RS2,
    Clk => Clk,
    A => R0,
    B => R1,
    C => R2,
    D => R3,
    E => R4,
    F => R5,
    G => R6,
    H => R7,
    Y => M2);

AdderSubtractor_0 : AdderSubtractor
PORT MAP(
    A => M2,
    B => M1,
    C_in => '0',
    Ctrl => OpSel,
    S => D,
    C_out => C_out,
    Zero => Zero,
    Overflow => Overflow);

Display_0 : Display
PORT MAP(
    A => R7,
    S_7Seg => S_7Seg);

process(Clk,Sel)
begin
    if (rising_edge(Clk)) then
        case M1 is
            when "0000" => JumpCheck <= '1';
            when others => Jumpcheck <= '0';
        end case;
    end if;
end process;

S <= R7;
end Behavioral;

```

Test Bench File

```
entity MicroProcessorSim is
-- Port ( );
end MicroProcessorSim;

architecture Behavioral of MicroProcessorSim is
COMPONENT MicroProcessor
    PORT( Res,Clk : in STD_LOGIC;
          S : out STD_LOGIC_VECTOR(3 downto 0);
          Zero, Overflow : out STD_LOGIC;
          S_7Seg : out STD_LOGIC_VECTOR (6 downto 0));
END COMPONENT;

SIGNAL Res, Clk : std_logic;
SIGNAL S : std_logic_vector(3 downto 0);
SIGNAL Zero, Overflow : std_logic;
SIGNAL S_7Seg : std_logic_vector(6 downto 0);
begin
UUT : MicroProcessor PORT MAP(
    Res => Res,
    Clk => Clk,
    S => S,
    Zero => Zero,
    Overflow => Overflow,
    S_7Seg => S_7Seg);

Clock : process
begin
    Clk <= '0';
    WAIT FOR 1 ns;

    Clk <= '1';
    WAIT FOR 1 ns;
end process;

process
begin
    Res <= '1';
    WAIT FOR 2 ms;

    Res <= '0';
    WAIT FOR 40 ms;

    Res <= '1';
    WAIT FOR 5 ms;

    Res <= '0';
    WAIT FOR 40 ms;
    WAIT;
end process;
end Behavioral;
```

Design Constraint File

```
## Clock signal
set_property PACKAGE_PIN W5 [get_ports Clk]
    set_property IOSTANDARD LVCMOS33 [get_ports Clk]
    create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports Clk]


##Buttons
set_property PACKAGE_PIN U18 [get_ports Res]
    set_property IOSTANDARD LVCMOS33 [get_ports Res]

## LEDs
set_property PACKAGE_PIN U16 [get_ports {S[0]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {S[0]}]
set_property PACKAGE_PIN E19 [get_ports {S[1]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {S[1]}]
set_property PACKAGE_PIN U19 [get_ports {S[2]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {S[2]}]
set_property PACKAGE_PIN V19 [get_ports {S[3]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {S[3]}]
set_property PACKAGE_PIN P1 [get_ports {Zero}]
    set_property IOSTANDARD LVCMOS33 [get_ports {Zero}]
set_property PACKAGE_PIN L1 [get_ports {Overflow}]
    set_property IOSTANDARD LVCMOS33 [get_ports {Overflow}]


##7 segment display
set_property PACKAGE_PIN W7 [get_ports {S_7Seg[0]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {S_7Seg[0]}]
set_property PACKAGE_PIN W6 [get_ports {S_7Seg[1]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {S_7Seg[1]}]
set_property PACKAGE_PIN U8 [get_ports {S_7Seg[2]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {S_7Seg[2]}]
set_property PACKAGE_PIN V8 [get_ports {S_7Seg[3]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {S_7Seg[3]}]
set_property PACKAGE_PIN U5 [get_ports {S_7Seg[4]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {S_7Seg[4]}]
set_property PACKAGE_PIN V5 [get_ports {S_7Seg[5]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {S_7Seg[5]}]
set_property PACKAGE_PIN U7 [get_ports {S_7Seg[6]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {S_7Seg[6]}]
```

TIMING DIAGRAMS


- 4-bit Add/Subtract unit

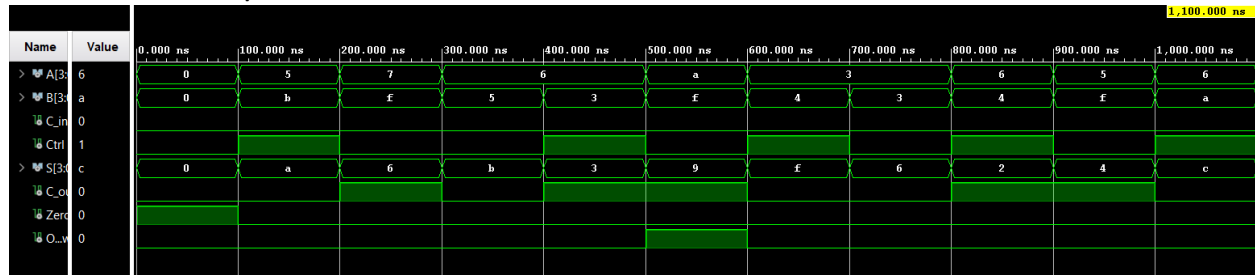


- 3-bit Adder

 

- 3-bit Program Counter (PC)

 


- 2-way 3-bit multiplexer

 


- 2-way 4-bit multiplexer




- 8-way 4-bit multiplexer

 


- Register Bank

 


- Program ROM

 


- Instruction Decoder

 

- Seven-Segment Display

 

- Micro Processor

 

CONCLUSION

- In the implementation of the 4 bit Add/Subtract unit, we can use an RCA with the input in two's complement form.
- When the subtract operation is called, invert the input that is to be subtracted and make the carry in signal into the first full adder '1'.
- 3 bit adder is implemented with only one 3 bit input because the purpose of the 3 bit adder is to increment the input by one. So the other input is set to '1'.
- 3 bit program counter has the duty of slowing the input signal and sending it out. In this case the signal is slowed by a factor of 50 million. It waits for 50 million clock cycles before sending the output signal.
- The three different multiplexers had to be clock synchronized, otherwise the output signal won't change during the instruction cycle.
- Unlike the other components without a clock connection like the instruction decoder or the adders where the inputs constantly change from one instruction to another, mux will have the same inputs until it passes through the signals. Hence they have to be clock synchronized.
- The register bank is implemented using d flip flops and R0 is hard coded to zero. The zero signal stored in R0 is used for the jump instructions.
- Program ROM was implemented by hardcoding the set of instructions. The ROM is limited to 8 instructions. The final instruction is kept empty to jump out of the internal loop when the conditions are met.
- A variety of buses had to be used when connecting the individual components to create the nano processor.

- The instruction decoder has two input signals and a lot of output signals. The inputs are the instruction from the ROM and the jump check signal.
- The jump check signal becomes one when the output of the first 8 way 4 bit mux becomes zero.
- This coupled with the instruction calling a jump, would raise the jump flag which is connected to the 2 way 3 bit mux which would then jump to the number specified in the instruction.
- The instruction decoder decides which registers to be selected when add/subtract operations are called.
- Similarly it decides which register to move a particular value to.
- Finally the nano processor component which is the combination of all the other components has two inputs as clock and the reset button.
- The reset button sets the program counter as well as all the registers in the register bank to zero.
- There are two outputs from the add/subtract unit denoting zero output and negative overflow.
- During the addition process in the add/subtract unit if two negative numbers are added which sums to more than negative eight, then the overflow bit becomes '1'.
- There is a output connected to the register R7. Which has a seven segment display also connected to it. 7 segment uses hexa-decimal representation.

CONTRIBUTION BY MEMBERS

210518H - K.S. RANASINGHE

- 4-bit Add/Subtract unit, 3-bit Adder, Program Counter, Instruction Decoder.

210170G - W.A.R.T FONSEKA

- All 3 mux components, Assembly code and Program ROM, Register Bank, 7-segment display.

Assembling of the components together and creating the nano processor was done by both of us together.

Basys simulation and corrections were also done together.

Formation of this lab report was also a joint work.

No. of hours spent was not measured. Given below is an estimate.

- K.S. RANASINGHE (210518H) = 5-6 hours
- W.A.R.T FONSEKA (210170G) = 5-6 hours